

mesago

pcim

6 – 8.5.2025
NUREMBERG, GERMANY

IISB² Topology for 48 V to 1 V Point of Load Applications

Dr.-Ing. Stefan Zeltner
Group Manager On-Board Converter
Fraunhofer IISB

Application example: Point of Load (PoL) DC/DC converter for Server & Memory in data centres

How much energy is needed?

2022


Gross elect. power consumption Germany 2022 ¹⁾	ca. 550 TWh
ICT energy demand ^{*)} in 2015... 2025 ²⁾	ca. 45 TWh
ICT infrastructure in Jahr 2022 ³⁾	ca. 24 TWh
power grid ³⁾	ca. 6 TWh
data centre ^{3) 4)}	ca. 18 TWh
Server & Memory ⁴⁾	ca. 11 TWh

2030

Estimated elect. power consumption 2030 ⁵⁾	ca. 655 TWh
Assumption for 2030: ICT needs ca. 10 % ^{**)}	ca. 65 TWh
ICT infrastructures in 2030 ³⁾	ca. 18... 30 ...58 TWh
power grid ³⁾	ca. 4 TWh
data centre ^{3) 4)}	ca. 26 TWh 32 TWh ⁶⁾
Server & Memory ⁴⁾	ca. 16 TWh 20 TWh ⁶⁾



relevant
for PoL

 

Example for a typ.
12 V → 1 V PoL
(2x 40 A_{cont.} units)

^{*)} Gebäudeversorgung, Öffentlichkeit, IKT Haushalte, IKT Arbeitsplatz, Telekommunikation, Rechenzentren

^{**)} with data from ²⁾

¹⁾ AGEB Energieverbrauch in Deutschland im Jahr 2023

²⁾ Stobbe et al.: Entwicklung des IKT-bedingten Strombedarfs in Deutschland, FhG IZM & Borderstep Institut, 2015

³⁾ Büro für Technologiefolgenabschätzung beim Deutschen Bundestag: Energieverbrauch der IKT-Infrastruktur, TAB-Fokus Nr. 35 zum Arbeitsbericht Nr. 198, 2022


⁴⁾ Bitcom e.V.: Rechenzentren in Deutschland Aktuelle Marktentwicklungen – Update 2023

⁵⁾ Pressekonferenz des Wirtschaftsministers Peter Altmaier am 13.7.2021


⁶⁾ Bitkom: Rechenzentren in Deutschland, Aktuelle Marktentwicklungen – Stand 2024

Application example: Point of Load (PoL) DC/DC converter for Server & Memory in data centres

 
**1x Rack $\approx$ up to 36x 800 W server nodes
with $\approx$ 36x20x PoL**



 **1x 800 W server node $\approx$ 2x CPU or 1x GPU
with $\approx$ 20x PoL**



 
**up to $\approx$ 400 A for CPU or $\approx$ 800 A for GPU
 $\approx$ 10x PoL for 1 CPU or 20x PoL 1 GPU**



to supply so many server nodes 48 V necessary
 $\rightarrow 230 V_{AC} \rightarrow 48 V_{DC} \rightarrow 12 V_{DC} \rightarrow 1 V_{DC}$

Application example: Point of Load (PoL) DC/DC converter for Server & Memory in data centres

 Typical approach: 2 conversion stages $48\text{ V} \rightarrow 12\text{ V}$ & $12\text{ V} \rightarrow 1\text{ V}$



Typical approach to save energy (by increasing efficiency)

→ **direct 48 V to 1 V conversion**

Many examples for direct 48 V to 1 V PoL solutions are known.



State-of-the-art solutions are based on topologies using a half-bridge and a current doubler rectifier.

Some problems:



- available area and volume
- costs
- voltage range necessary
- high dynamic requirements

Efficiency values are strongly depending on load current. The values shown here are for $\approx 25\text{ A}$ of a $40\text{ A}_{cont.} / 60\text{ A}_{max.}$ PoL unit what represents a typ. server load of ca. 63%.

  State-of-the-art 2-stage and 1-stage approaches




2-stage approach

  


1-stage approach

State-of-the-art 2-stage approach

1x 48 V → 12 V

 


plus 20x 12 V → 1 V

 

2-stage solution			1-stage solution			Ratio 1-stage/ 2-stage
Qty	1x 48V/12V + 20x 12V/1V, 40A → 800A @ 1V	Sum	Qty	16x 48V/1V, 50A → 800 A @ 1V	Sum	
4	EPC 2619 100 V, 4.2 mOhm, GaN; Die: 2.5x1.5 mm	15 mm ²	16	LMG5200 80 V, 15 mOhm, GaN (6x8 mm); est. 3.6x less area due 3.6x higher Rdson →2x(2.5x1.5) /3.6 =2.1 mm ² +2.5 mm ³ for driver	16x 4.6 mm ² =74 mm ²	74/ (15+5+ 56+2+ 10) =0.84≈1
2	UP1966P (pri. Gatedriver); Die ca. 1.6x1.6 mm	estim. 5 mm ²	-	-	-	
6	EPC 2067 40 V 1.55 mOhm; Die: 2.85 x 3.25 mm	56 mm ²	-	-	-	
2	LMG1020 (sec. Gatedriver) Die Size: ?	estim. 2 mm ²	-	-	-	51/10 = 5.1
1	dsPIC33CK64MP 105 FAMILY in 4x4 mm Package	estim. 10 mm ²	-	-	-	
1	Transformer 3:1:1 for 83 A @ 12 V with 2x ML91S and 4x ML95S Ferrit cores @ ca. 1.6 MHz	estim. 10 g	16	Transformer 5:1 for 50 A @ 1 V with 2x ER18/3.2/ 10-3F36-S Ferrit cores @ 600 kHz	16x 3.2 g =51 g	
14	22 nF resonant capacitor	-	-	-	-	0.325 /16 /(1.6/20) = 0.25
20	e. g. MP86957 BOT MOSFET ca. 1.6 mOhm, Si (6x5 mm)	-	16x 4 =64	4x EPC2023 30 V, 1.3 mOhm, GaN (6.05x2.3 mm)	-	
20	e.g. PGL6076.131 130 nH max. 60 A, 0.16 mOhm @ 500 kHz (7.6x7.6x12 mm)	-	16x 2 =32	e.g. Würth 744308025, 250nH, 27 A, 0.37 mOhm, (10x7x6.8 mm)	-	


State-of-the-art 1-stage approach

16x 48 V → 1 V

 


State-of-the-art 2-stage approach

1x 48 V → 12 V

 



plus 20x 12 V → 1 V

 


2-stage solution			1-stage iib ² solution			Ratio 1-stage/ 2-stage
Qty	1x 48V/12V + 20x 12V/1V, 40A → 800A @ 1V	Sum	Qty	20x 48V/1V, 40A → 800 A @ 1V	Sum	
4	EPC 2619 100V, 4.2 mOhm, GaN; Die: 2.5 x 1.5 mm	15 mm ²	20	LMG5200 80V, 15 mOhm, GaN (6x8 mm); estim. 3.6x less area due 3.6x higher R _{dson} → 2x(2.5x1.5)/3.6 = 2.1 mm ² + 2.5 mm ² for driver	20x 4.6 mm ² = 92 mm ²	92/(15+5+56+2+10) = 1.05 ≈ 1
2	UP1966P (pri. Gatedriver); Die ca. 1.6 x 1.6 mm	estim. 5 mm ²	-	-	-	
6	EPC 2067 40V 1,55 mOhm; Die: 2.85 x 3.25 mm	56 mm ²	-	-	-	-
2	LMG1020 (sec. Gatedriver) Die Size: ?	estim. 2 mm ²	-	-	-	-
1	dsPIC33CK64MP 105 FAMILY in 4x4 mm Package	estim. 10 mm ²	-	-	-	-
1	Transformer 3:1:1 for 83 A @ 12 V with 2x ML91S and 4x ML95S Ferrit cores @ 1.6 MHz	estim. 10 g	20	Transformer 6:1 for 50 A @ 1 V with R16x9.6x6.3, N49 @ 410 kHz	20x 3.7 g = 74 g	74/10 = 7.4
14	22 nF resonant capacitor		20	150 nF resonant capacitor		20/14 = 1.4
20	e. g. MP86957 BOT MOSFET ca. 1.6 mOhm, Si (6 x 5 mm)		20x 2 = 40	e. g. MP86957 BOT MOSFET ca. 1.6 mOhm, Si (6x5 mm)		(1.6/40)/ (1.6/20) = 0.5
20	e.g. PGL6076.131 130 nH max. 60 A, 0.16 mOhm @ 500kHz (7.6x7.6x12 mm)		20x 2 = 40	e.g. PGL6076.131 130 nH max. 60 A, 0.16 mOhm @ 410 kHz possible with 2x 30 A inductors		40/20 = 2 40*0.5/20 = 1

1-stage IISB² approach

20x 48 V → 1 V

  


Direct comparison

 

State-of-the-art 1-stage approach


48 V $\rightarrow$ 1 V

 


1-stage IISB² approach

(integrated, galvanically isolated, separated buck/boost topology)


48 V $\rightarrow$ 1 V

 

 Application example: Point of Load (PoL) DC/DC converter for Server & Memory in data centres



≈ 1.6 mOhm
for LS MOSFET

 


Advantage:
+2% efficiency compared with typ. 2-stage approach (as expected).

But compared with 1-stage state-of-the-art hard-switched half-bridge with current doubler rectifier using 2x 30 V GaN with 1.3 mOhm parallel = 0.65 mOhm

less semiconductor area needed
≈ 50% *)

iisb² topology works with only
≈ 1.6 mOhm for LS MOSFET

 *) if same semiconductor technology is used



mesago

pcim

6 – 8.5.2025
NUREMBERG, GERMANY

Thank you for the attention!

I'm pleased to answer your
questions.
stefan.zeltner@iisb.fraunhofer.de

Messe Frankfurt Group